



IP PARIS



# Synchronous sequential logic

ECE\_3TC31\_TP/INF107

Tarik Graba   Ulrich Kühne   Guillaume Duc  
2023-07





# Introduction

## Combinational logic

- The output of a function depends only on the present value of the inputs
  - For the same values of the inputs, the output is *a/ways* the same
- It is used to build logic and arithmetic operators

## Combinational vs. Sequential logic

  

Which timing diagram cannot be produced by combinational logic?


## Combinational vs. Sequential logic

With sequential logic, the output of a function depends on:

- the present value of its input signals
- and on the sequence of past inputs


The function has a state (or memory)

## How to deal with propagation time

 


- The propagation time  $t_p$  is not null
- During this time
  - **The output ( $S$ ) is not valid**
  - **The inputs ( $E_0, E_1, E_2$ ) must not change**
- How to chain computations (i.e. perform  $F(E_0, E_1, E_2)$  then  $F(E'_0, E'_1, E'_2) \dots$ )?

## How to deal with propagation time

 

- We maintain the inputs values ( $E_0, E_1, E_2$ ) stable for at least  $t_p$
- By adding a memory component that
  - samples (updates  $E_0, E_1, E_2$  from the values of its inputs  $E_{i/0}, E_{i/1}, E_{i/2}$ )
  - memorises (keep the values of  $E_0, E_1, E_2$  stable as long as it is needed)

## How to deal with propagation time

 


### ■ Once the results is available

- The output  $S$  is sampled
- The inputs  $E_{i0}, E_{i1}, E_{i2}$  can sample new values at the same time
- The output  $S_o$  is memorised and can be used in another computation




## How to deal with propagation time

 

- We use the same signal to **synchronize** sampling in all the flip-flops: **the clock** ( $clk$ )

## How to deal with propagation time

 


# D flip-flop

## D flip-flop

- D flip-flop (dff, register...)
- Input: **D**
- Output: **Q**
- Clock input: **clk**
 
### Operation


- When the clock **clk** goes from 0 to 1 (*rising edge*), the value of the input **D** is captured and copied to the output **Q** (*sampling*)
- The rest of the time, the value of the output **Q** does not change (*memorization*)



## Truth table


		D	clk	Q	Operation
0	↑	0			D is copied to Q ( <i>sampling</i> )
1	↑	1			D is copied to Q ( <i>sampling</i> )
×	0	Q			Q keeps its value ( <i>memorization</i> )
×	1	Q			Q keeps its value ( <i>memorization</i> )
×	↓	Q			Q keeps its value ( <i>memorization</i> )

## Exercise

 


Complete this timing diagram

## Correction

 


## Exercise

 


Complete this timing diagram



## Correction

 


## Timing constraints

 


- The input must be stable around the rising edge of the clock
  - The value must be stable  $t_{su}$  before the edge (*setup*)
  - The value must be kept stable  $t_h$  after the edge (*hold*)
- There is a delay  $t_{co}$  (*clock to output*) for the data to be stable at the output
 
## Register

- A **register** is a set of flip-flops used in parallel
- Example: a 4-bit register



## Shift register

 


- Works because  $t_{co}$  is always greater than  $t_h$
- A shift register can delay a signal by a number of clock cycles

## Synchronous Logic Design Rules

- All combinational blocks are surrounded by flip-flops/registers
- All D flips-flops are synchronous
  - They use the same clock signal
  - The rising edge of the clock signal must arrive at the same time
  - No combinational operations on the clock signal
- The clock period must be compatible with the propagation time in combinational logic

## Timings in Synchronous Logic

 

For synchronous sequential block to behave correctly, the following constraint must be satisfied:

$$T_{clk} > t_{co} + t_p + t_{su}$$

If this timing constraint is not respected, the sampled value may be incorrect.

## Timings in Synchronous Logic

$$T_{clk} > t_{co} + t_p + t_{su}$$

This constraint must be satisfied for all combinational paths between two flip-flops.

We define  $t_{crit}$  as the propagation delay in the longest combinatorial path (critical path).

$$T_{clk} > t_{co} + t_{crit} + t_{su}$$

We can express the maximum working frequency as:

$$F_{max} = \frac{1}{t_{co} + t_{crit} + t_{su}}$$





## Initialization

- At power-up, the value of the output of a D flip-flop is not predictable (no initial value).
- An external signal must be used to force this value: the **reset** signal (the output is forced to 0).
- Two types of reset signal can be used: asynchronous and synchronous.



  
## Asynchronous reset

- **Asynchronous** reset: its action is independent of the clock
- It is a special input of D flip-flops
- Can be active on a high-level (positive reset, when the reset is equal to 1) or a low-level (negative reset, when the reset is equal to 0)


 
## Synchronous reset

- **Synchronous** reset: it is only effective on rising edges of the clock






## Synchronous reset

How to build a D flip-flop with a synchronous reset using a normal D flip-flop and logic gates?

## Synchronous reset

 


## Synchronous sequential logic: summary

- D flip-flops used on inputs and outputs of combinational logic blocks
- One global clock connected directly to all the flip-flops
- The initial state of flip-flops is forced by an global external signal: the reset

# Applications

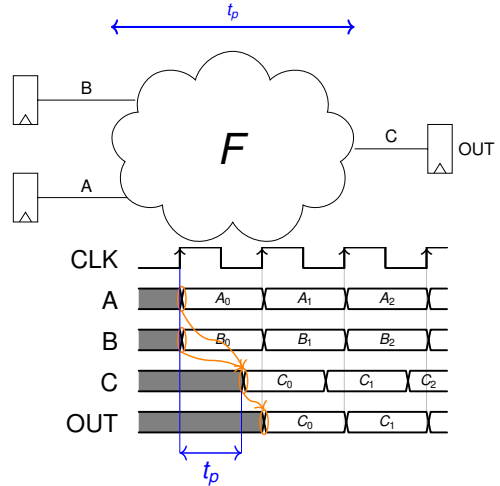
## Pipeline

- $F$  is a combinational function with a propagation delay of  $t_p$
- Constraint:  $T_{clk} > t_{co} + t_p + t_{su}$


 
## Pipeline


- We decompose  $F$  in two combinational functions  $F_1$  and  $F_2$  (propagation delays  $t_{p1}$  and  $t_{p2}$ )
- We suppose that  $t_{p1} < t_p$  and  $t_{p2} < t_p$
- Constraint:  $T_{clk} > t_{co} + t_{p1} + t_{p2} + t_{su}$




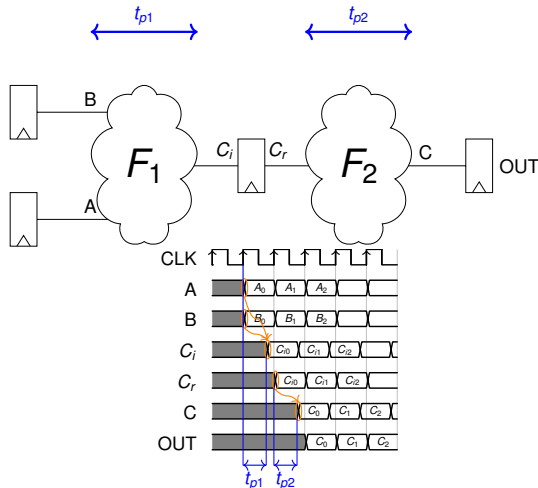
## Pipeline

- We can introduce a D flip-flop between  $F_1$  and  $F_2$ 
  - We call this a *register barrier*.
- Constraint:  $T_{clk} > t_{co} + t_{p1} + t_{su}$  and  $T_{clk} > t_{co} + t_{p2} + t_{su}$
- If  $t_{p1} < t_p$  and  $t_{p2} < t_p$ 
  - we can reduce the clock period (increase the clock frequency)





## Pipeline

- The pipeline is a method to increase the clock frequency of a circuit
- The size of the circuit is increased (modification of the combinational logic, addition of flip-flops)
- The initial latency is increased